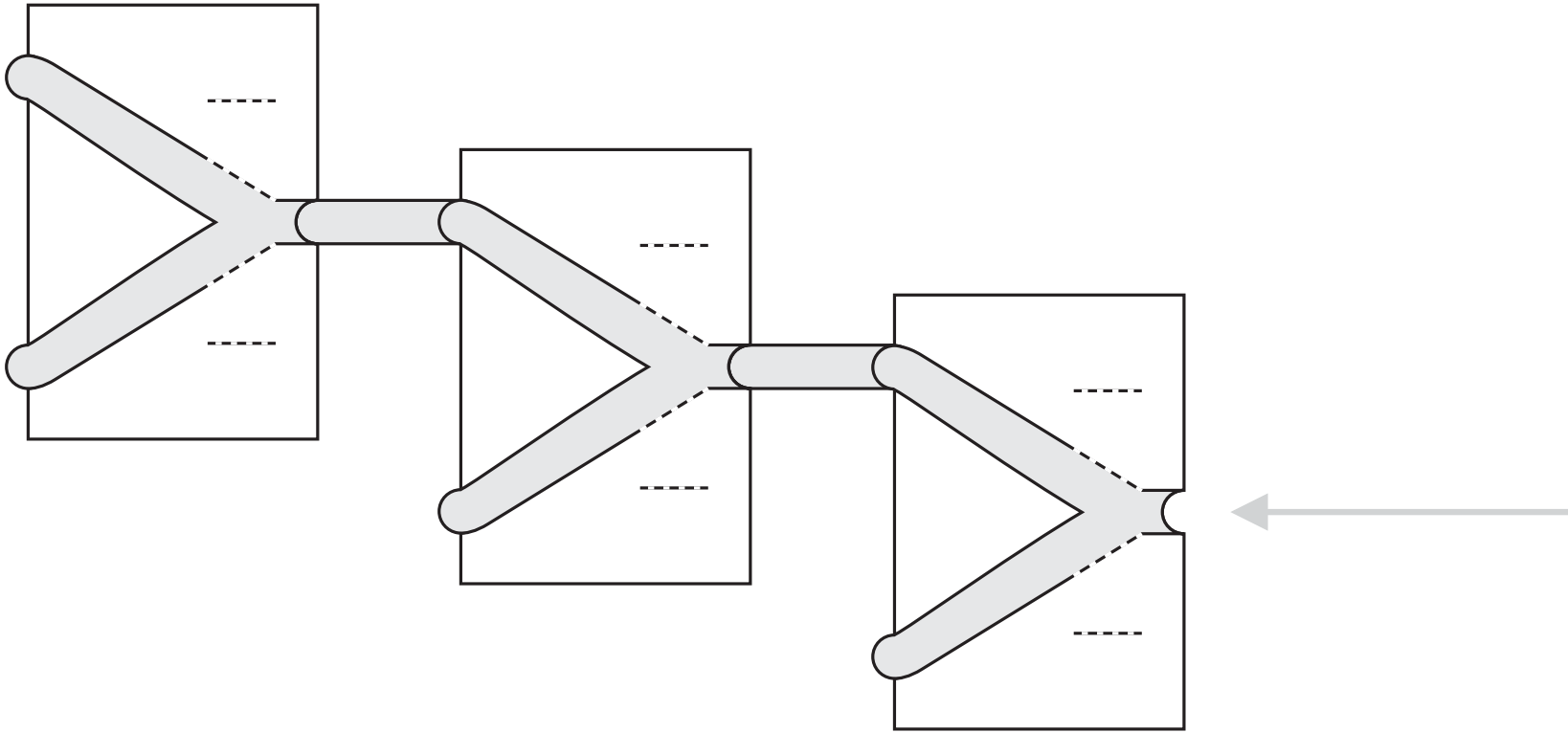


Numbers take place

Try out the switching and write down the states of the Flip-Flops in the table below. What do you notice? How does it continue?



0		0		0	Starting condition
					1. run-through
					2. run-through
					3. run-through
					4. run-through
					5. run-through
					6. run-through
					7. run-through

In order to get Flip-Flops that work, you have to plug in the handles, you have to plug in the handles. Cut along the four dotted lines of each Flip-Flop and cut out the handles. Put them through the slits of the Flip-Flops so that the tracks of the handles are above the tracks of the Flip-Flops. Remember: whenever you move through a Flip-Flop, you have to switch over the handle. It could be best to work with both hands: one for moving through the Flip-Flops, the other for switching over the handles.

